

ECE-301-204

Lab5 Combinational Logic Circuit Design

Marcus Domingo

03/02/2016

Objective:

To design and implement a circuit that detects all of the Fibonacci numbers between 0 and 15.

Materials and Equipment:

- ET-1000 Trainer
- Wires
- Breadboard
- 1 74xx04 (NOT gates), 1 74xx08 (AND gates), 1 74xx32 (OR gates)

Laboratory Data:

| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>f</i> |
|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |


This is the truth table for the Fibonacci number from 0 to 15. The numbers that result in “1” are those of the Fibonacci series which are 0,1,2,3,5,8,13. From this we can design a Karnaugh map for the truth table.

| | | AB | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| CD | 00 | 1 | 0 | 0 | 1 |
| | 01 | 1 | 1 | 1 | 0 |
| | 11 | 1 | 0 | 0 | 0 |
| | 10 | 1 | 0 | 0 | 0 |


$$f = \bar{A} \cdot \bar{B} + B \cdot \bar{C} \cdot D + \bar{B} \cdot \bar{C} \cdot \bar{D}$$

$$f = \bar{A} \cdot \bar{B} + \bar{C}(B \cdot D + \bar{B} \cdot \bar{D})$$

 Above is the Karnaugh map for the Fibonacci number truth table along with the SOP function that satisfies the Karnaugh map.



 Above is a mapped out design for the logic circuit that will produce the Fibonacci numbers 0 to 15. Below is the physical circuit that was built from the above diagram.



Comments and Conclusions:

This lab gave us practice using 4 variable Karnaugh maps based off of a truth table that follows the rules of a common mathematical sequence. We also minimized the inputs on some of the gates from 3 to 2 using factoring on the SOP function. This allowed us to use less IC's than we would have used if we needed a 3 input gate.