

ECE 301 Digital Electronics
Multiplexers
Revised Fall 2013
K. Hintz & C. Lorie

OBJECTIVE

To understand the operation of an 8x1 multiplexer (MUX) and design and verify the correct operation of a 4x2 MUX.

PREPARATION

Design and construct the circuits.

PROCEDURE

1. With reference to the datasheet for a 74LS151, verify that the eight-input MUX behaves in accordance with the truth table that is included on the first page of the datasheet.
2. A two by four (2x4) input multiplexer has two sets of inputs labeled A and B , each of which is 4-bits wide. There is one 4-bit wide output.
 - When the selector input, A/\bar{B} , pronounced "A B-bar" is set to a logic 1, then the four A inputs, A_1 through A_4 are routed to the four output bits, O_1 through O_4 .
 - When the selector input, A/\bar{B} is set to a logic 0, then the four B inputs, B_1 through B_4 are routed to the four output bits, O_1 through O_4 .

note: The identifier for the selector input, A/\bar{B} , is a standard terminology which incorporates the polarity of the activating signal in the identifier. That is, when the selector is asserted as a logic 1, the A input is passed to the output. In some cases it may be desirable to use what is called negative logic where the A input is asserted as a zero, that is a zero on the selector input would cause the A inputs to pass to the output. In this case, the proper identifier for the selector input would be \bar{A}/B . This type of identifier avoids any misinterpretation about the polarity of the actuating signal.

- a. Design a 4x2 MUX by specifying its truth table.
- b. Design a circuit to implement the truth table of the 4x2 MUX.
- c. Build and verify the correct operation of the MUX by comparing the truth table to the behavior of the circuit.
 - Apply all ones to the A data inputs.
 - Apply all zeros to the B data inputs.
 - Apply ones to the even numbered A data inputs, and zeros to the odd numbered A data inputs. Simultaneously apply ones to the odd numbered B data inputs, and zeros to the even numbered B data inputs. Verify that each output bit toggles when the A/\bar{B} selector input is toggled (changed from one value to another)