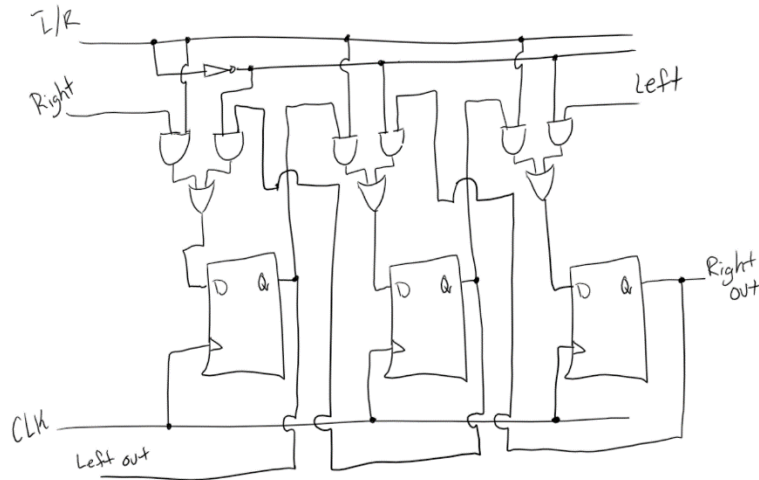


7.13:



7.18: The count starts out at 000, then input into T0 is a 1 so the count is 001. Then output of 1 goes to T1, while input of 1 goes into T0 so the count is then 010. Then the output of 1 goes to T2, while output of 0 goes to T1, while input of 1 goes to T0 so the count is 111. Then back to 000. Therefore, the counting sequence for the counter is 000, 001, 010, 111.

7.37: $t_{su} = 0.6 \text{ ns}, t_h = 0.4 \text{ ns}, 0.8 \text{ ns} \leq t_{cq} \leq 1.0 \text{ ns}$

$$T_{min} = t_{cq} + 3(t_{AND}) + t_{XOR} + t_{MUX} + t_{su} = 1.0 + 3(1.2) + 1.2 + 7.0 + 0.6 = 13.4 \text{ ns}$$

$$F_{max} = \frac{1}{T_{min}} = \frac{1}{13.4 \text{ ns}} = 74.63 \text{ MHz}$$

7.38: $T_{min} = t_{cq} + k(t_{REG}) + t_{MUX} + t_{su}$

$$F_{max} = \frac{1}{T_{min}} = \frac{1}{t_{cq} + k(t_{REG}) + t_{MUX} + t_{su}}$$

8.29:


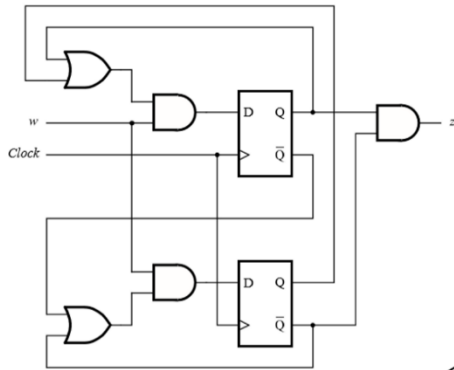


Figure P8.2 Circuit for problem 8.29.

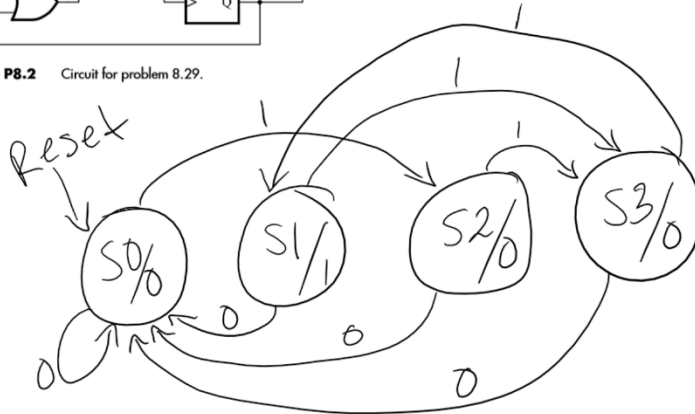

Present State	Next State		Output z
	w = 0	w = 1	
S0	S0	S2	0
S1	S0	S3	1
S2	S0	S3	0
S3	S0	S1	0

6.

$$Q^+ = JQ + K'Q$$

$$J = \overline{(X'B)} \overline{(XB)} = (X+B)(X'+B) = X'B + XB'$$

$$K = \overline{X'B} = X'B$$

$$A^+ = (X'B + XB')A' + X'BA = X'BA' + X'BA + X'B'A' = X'B + X'BA'$$

$$J = K = \overline{X' + A'} = XA$$

$$B^+ = XAB' + XAB = XA$$

First JK flip-flop:




Inputs		Current State	Next State
X	B	A	A*
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Second JK flip-flop:

Inputs		Current State	Next State
X	A	B	B*
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Output
Z
1
1
0
0
0
1
0
0

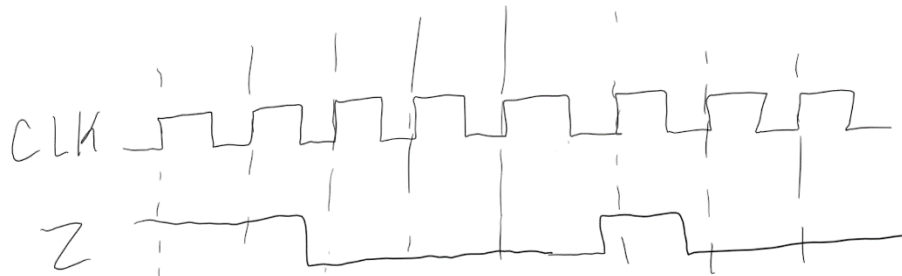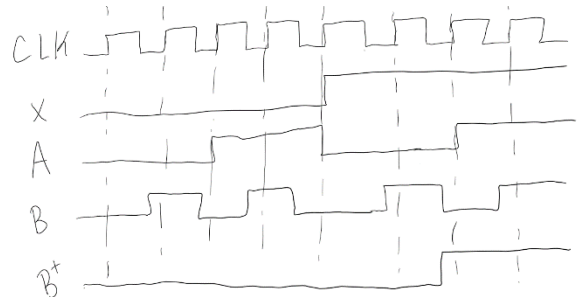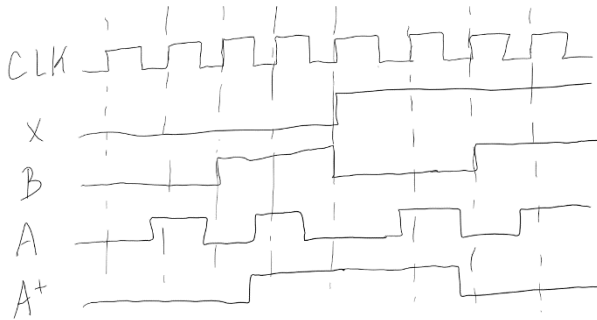The circuit is a Moore machine because the output depends on the current state only.



7.

$$J_1 = XQ_2' \quad K_1 = X$$

$$Q_1^+ = XQ_2'Q_1' + XQ_1$$

$$J_2 = XQ_1 \quad K_2 = X$$

$$Q_2^+ = XQ_1Q_2' + XQ_2$$

First JK flip-flop:

Inputs		Current State	Next State
X	Q2	Q1	Q1*
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Second JK flip-flop:

Inputs		Current State	Next State
X	Q1	Q2	Q2*
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Output
Z
0
0
0
0
1
0
0
0

This circuit is a Mealy machine because the output depends on the current state and input.

