

ECE 301 Digital Electronics
Flip-Flops and Frequency Dividers
Revised Fall 2013
K. Hintz & C. Lorie

OBJECTIVE

To understand the operation of D and JK Flip-flops.

To understand the usage of a flip-flops as clock signal dividers.

BACKGROUND

It is common in digital circuits to synchronize the behavior of the individual logic circuits through the use of a particular signal, generally not considered a data input, called a clock. A clock is generally a square wave, but some systems use a non-symmetric clock. It is also common to have clocks of various frequencies applied to the circuits, usually multiples (or more commonly divisors) of the base clock by 2^n . A simple way to do this is to apply the output of a D-FF back to its D-input as is done in this lab. This will divide the input clock frequency by a factor of 2. Additional divisions of the clock frequency can be done by cascading the output of one FF with the D-input of the next.

PREPARATION

Design and construct the circuits.

PROCEDURE

- 1) Using a D flip-flop (74LS74), build a divide the clock frequency by 2 circuit by connecting Q output to the D input. The frequency/2 is output at the Q output.
 - Use the square wave signal from the trainer to provide the clock signal and display the operation of the circuit on your trainer lights, *i.e.*, connect one light to the clock signal and another to the Q output.
 - Remember to include the clear and preset inputs to the FF as part of your circuit design.
- 2) Repeat part 1) above using a JK flip-flop (74LS76...be careful to note the non-standard pins for GND and V_{cc} as shown at the top of page 2 of the datasheet).
 - For this type of flip-flop, connect a trainer light to the non-inverting output, Q , and another trainer light to the clock input.
 - Note that there are two possible configurations of the J and K inputs that will cause the flip-flop to divide the input clock by two. Do both configurations work correctly?