

Adder Circuits

Revised Fall 2013

K. Hintz & C. Lorie

OBJECTIVE


To build and verify the correct operation of a Half Adder, a Full Adder, and a 2-bit Ripple Carry Adder.

PREPARATION


1. Construct the truth table for the Half Adder. (**inputs:** A, B; **output:** Sum)
2. Construct the truth table for the Full Adder. (**inputs:** A, B, C_{in} ; **outputs:** Sum, C_{out})
3. Draw a block diagram for a 2-bit Ripple Carry Adder (from two 1-bit Full Adders).

PROCEDURE

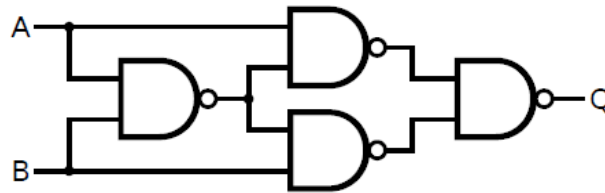1. Design and build a Half Adder using five NAND gates only.
Hint: An XOR gate can be realized using four NAND gates as illustrated below



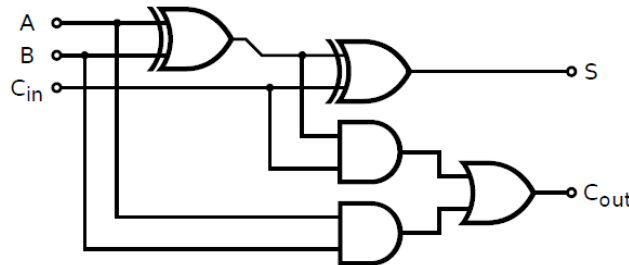2. Design and build a Full Adder using two XOR gates, two AND gates, and one OR gate.



3. Design and build a 2-bit Ripple Carry Adder.
 - a. Build a second Full Adder (using the same set of gates as in part 2).
 - b. Connect the two Full Adders to realize the 2-bit Ripple Carry Adder.
4. Demonstrate the correct operation of all adder circuits to the TA. The adder circuits should work for all combinations of the inputs.