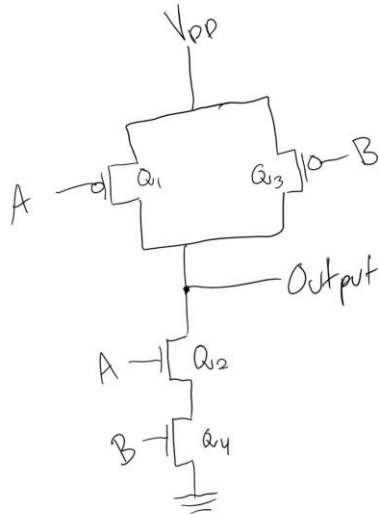


1. AND gate CMOS:




2. Function table for the give CMOS circuit:

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6	F
0	0	0	ON	OFF	ON	OFF	ON	OFF	0
0	0	1	ON	OFF	ON	OFF	OFF	ON	0
0	1	0	ON	OFF	OFF	ON	ON	OFF	0
0	1	1	ON	OFF	OFF	ON	OFF	ON	0
1	0	0	OFF	ON	ON	OFF	ON	OFF	0
1	0	1	OFF	ON	ON	OFF	OFF	ON	0
1	1	0	OFF	ON	OFF	ON	ON	OFF	0
1	1	1	OFF	ON	OFF	ON	OFF	ON	1

3. Given input analyzation of the given CMOS circuit:

A	B	C	D	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	F
0	0	1	0	ON	OFF	ON	OFF	OFF	ON	ON	OFF	1
0	1	0	0	ON	OFF	OFF	ON	ON	OFF	ON	OFF	0
1	1	0	0	OFF	ON	OFF	ON	ON	OFF	ON	OFF	1

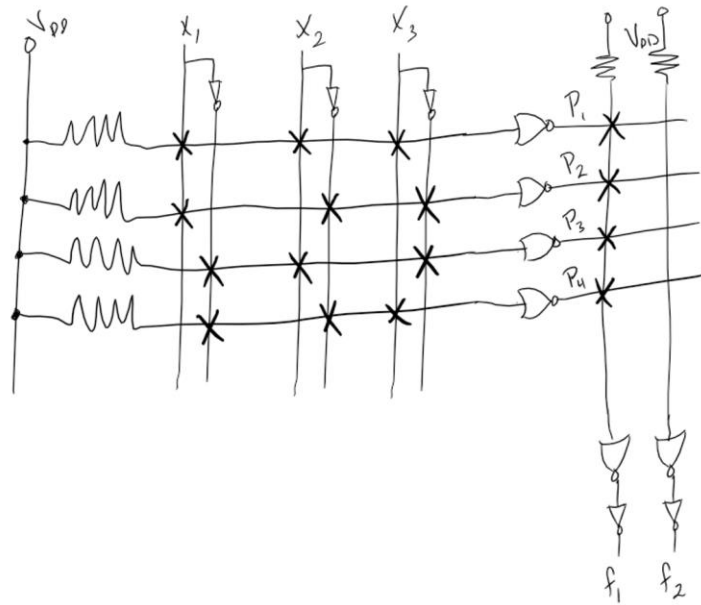4. 3.37: $f_1(x_1, x_2, x_3) = \sum m(0,3,5,6) = \overline{x_1}\overline{x_2}\overline{x_3} + \overline{x_1}x_2x_3 + x_1\overline{x_2}x_3 + x_1x_2\overline{x_3}$



5. 3.39:

